

名列番号

氏名 秋田 純一


1(1)

(中略)

$$V_o = -\frac{R_2}{R_1} V_i$$

⑤
念中
回路の
→ A
③

1(2)

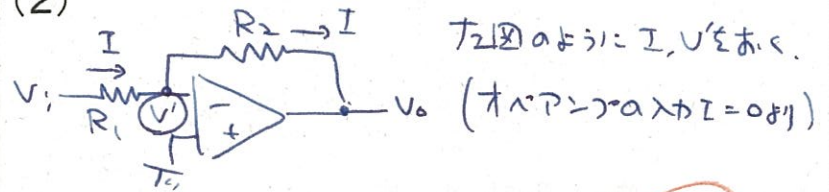


$$\begin{cases} I = \frac{V_i - V'}{R_1} = \frac{V' - V_o}{R_2} \\ V_o = -A V' \end{cases}$$

∴

$$V_o = \frac{-A R_2}{R_1 + R_2 + A R_1} V_i$$

⑩
⑮
文字の
定数
→ A → ⑩

1(3)

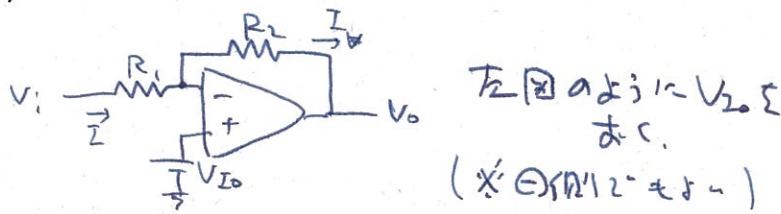

仮起の -I. ①側の電圧は VZo.

①) ①側から

$$I = \frac{V_i - V_{Zo}}{R_1} = \frac{V_{Zo} - V_o}{R_2}$$


$$\therefore V_o = \frac{-R_2 V_i + (R_1 + R_2) V_{Zo}}{R_1}$$

⑩
⑮
念中
→ A → ⑩

1(4)

$V_i: 0 \rightarrow 5V$ ②: $V_o: 0 \rightarrow -10V$.

V_i, V_o のグラフは左の通り.

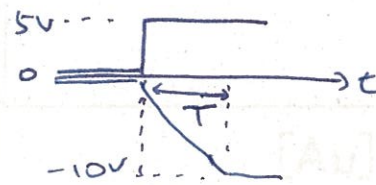

$2k-c-t = 10V/\mu s$ ①

$$T = 1\mu s$$

⑩
⑮ → A
念中
0.5μs → A

2(1)

(中略)

$$V_o = \frac{A}{1 + A\beta} V_i$$

⑤

2(2)

$$\begin{aligned} 20 \log_{10} 300,000 \\ = 20 (\log_{10} 3 + \log_{10} 10^5) \\ = 20 (0.5 + 5) \\ = 110 \text{ [dB]} \end{aligned}$$

⑤

2(3)

一次遅滞の定数

$$f_c = 20 \text{ [Hz]}$$

⑤

2(4)

$$A = \frac{A_{dc}}{1 + j f/f_c} \quad \text{②か③}$$


$$|A| = \frac{A_{dc}}{1 + A_{dc}\beta} \cdot \frac{1}{\sqrt{1 + (f/f_c)^2}}$$

∴ ①) ②) の回路の $f_c (1 + A_{dc}\beta)$

$$\begin{aligned} \text{代入} \quad 20(1 + 3 \times 10^5 \times 0.1) \\ \approx 20 \times 3 \times 10^4 = 6 \times 10^5 \text{ [Hz]} \\ (600 \text{ kHz}) \end{aligned}$$

⑮

3(1)

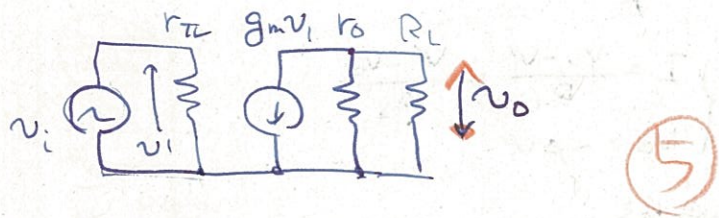

3(2)


(15')

$$v_o = -g_m v_i (R_L / R_L)$$

$$\therefore A_v = \frac{v_o}{v_i} = -g_m (R_L / R_L)$$

(5)

3(3)

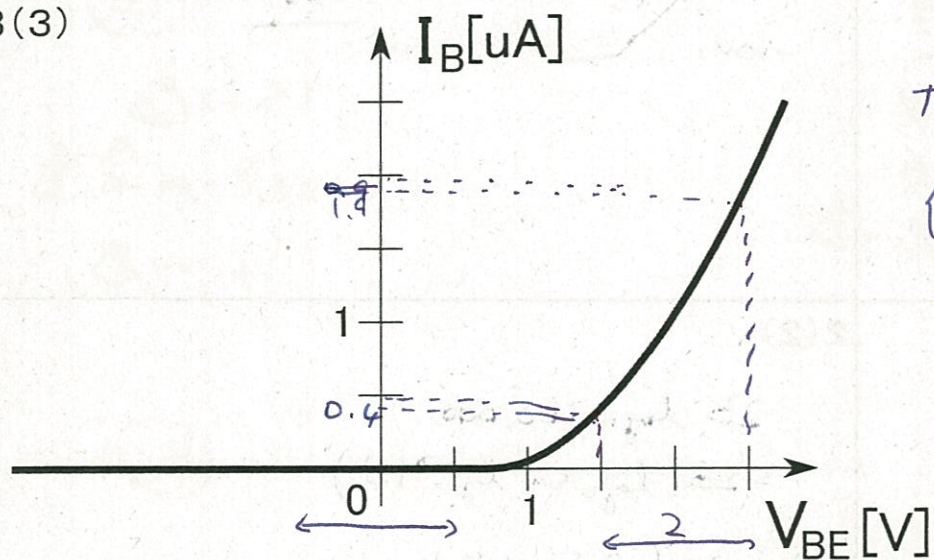

T_2 (15')

$$\begin{cases} V_{BIAS} = 0V \rightarrow 0 \sim 0 \mu A \\ V_{BIAS} = 2V \rightarrow 0.4 \sim 1.9 \mu A \end{cases}$$

(5)
(5)

4

(15)

基本 (15) + d