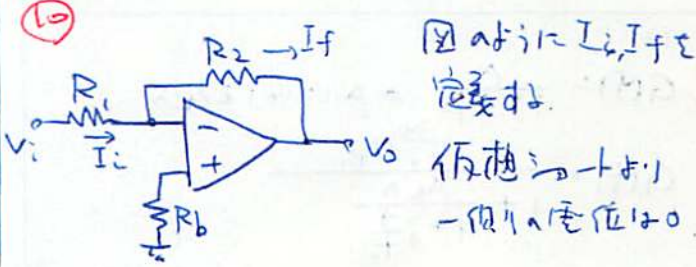


名列番号 \_\_\_\_\_

名前 秋田 隼

1. (1)




$$\therefore I_i = \frac{V_i}{R_1}, \quad I_f = \frac{V_o}{R_2}$$

オペアンプの入力には電流は流れないので  
 $I_i = I_f$

$$\therefore V_o = -\frac{R_2}{R_1} V_i$$

文法上の定数値  
→  $\Delta$   $\Delta$

1. (3)

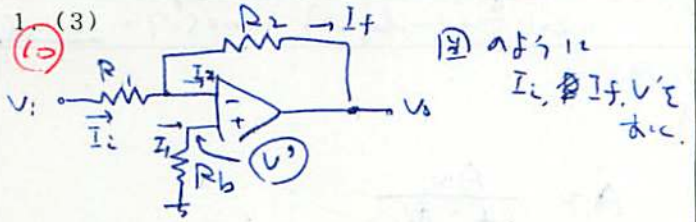

$$V' = -R_b I_1, \quad I_i = I_f + I_2$$

$$I_i = \frac{V_i - V'}{R_1}, \quad I_f = \frac{V' - V_o}{R_2}$$

したがって

$$\frac{V_i + R_b I_1}{R_1} = -\frac{R_b I_1 + V_o}{R_2} + I_2$$

$$-\frac{R_2}{R_1} (V_i + R_b I_1) = R_b I_1 + V_o - R_2 I_2$$

$$\therefore V_o = -\frac{R_2}{R_1} V_i + R_2 I_2 - \left(\frac{R_2}{R_1} + 1\right) R_b I_1$$

1. (4)

$$R_b = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} \quad \left( \frac{I_{off}}{V_i} \right)$$

$$V_o = -\frac{R_2}{R_1} V_i + R_2 I_2 - R_2 I_1$$

$$= -\frac{R_2}{R_1} V_i + R_2 (I_2 - I_1)$$

$$= -\frac{R_2}{R_1} V_i + R_2 I_{off}$$

1. (2)

⑩ ①②: - 側の電圧 \$V'\$ と \$V\_o\$ との関係

$$V_o = A(-V') = -AV'$$

$$I_2 = \frac{V_i - V'}{R_1} = I_f = \frac{V' - V_o}{R_2}$$

したがって

$$V_i + \frac{V_o}{A} = -\frac{R_1}{R_2} \left(1 + \frac{1}{A}\right) V_o$$

$$V_i = \left\{ -\frac{R_1}{R_2} \left(1 + \frac{1}{A}\right) - \frac{1}{A} \right\} V_o$$

$$\therefore V_o = -\frac{1}{\frac{R_1}{R_2} \left(1 + \frac{1}{A}\right) + \frac{1}{A}} V_i$$

2. (1)

⑩ A が \$V\_o\$ と \$V'\$ との関係

$$V' = V_i - \beta V_o, \quad V_o = AV'$$

$$\therefore V_o = A(V_i - \beta V_o) = AV_i - A\beta V_o$$

したがって

$$V_o = \frac{A}{1 + A\beta} V_i \quad \text{よって } G(F) = \frac{A}{1 + A\beta}$$

電子回路第1および演習 期末試験 解答用紙(裏面)

2. (2)  $\text{計算} \rightarrow \text{④} \rightarrow \text{③}$

$$A_{dc} = 20 \log_{10} 500000 = 20(5 + \log_{10} 5)$$

$$= 20(5 + 1 - \log_{10} 2) = 20 \times 5.7 = \underline{114 \text{ dB}}$$

2. (3)

$$f_1 = 10 \text{ Hz}$$

2. (4)

$$A = \frac{A_{dc}}{1 + j f/f_1}$$

2. (5)

$$G(f) = \frac{A}{1 + A\beta}$$


$$G(f) = \frac{\frac{A_{dc}}{1 + j f/f_1}}{1 + \frac{A_{dc}\beta}{1 + j f/f_1}}$$

$$= \frac{A_{dc}}{1 + j f/f_1 + A_{dc}\beta} \left( \frac{1 + j f/f_1}{1 + j f/f_1} \right)$$

$$= \frac{A_{dc}}{(1 + A_{dc}\beta) + j f/f_1}$$

$$= \frac{\frac{A_{dc}}{1 + A_{dc}\beta}}{1 + j \frac{f}{f_1(1 + A_{dc}\beta)}} \quad \delta'$$

より  $f_1(1 + A_{dc}\beta)$

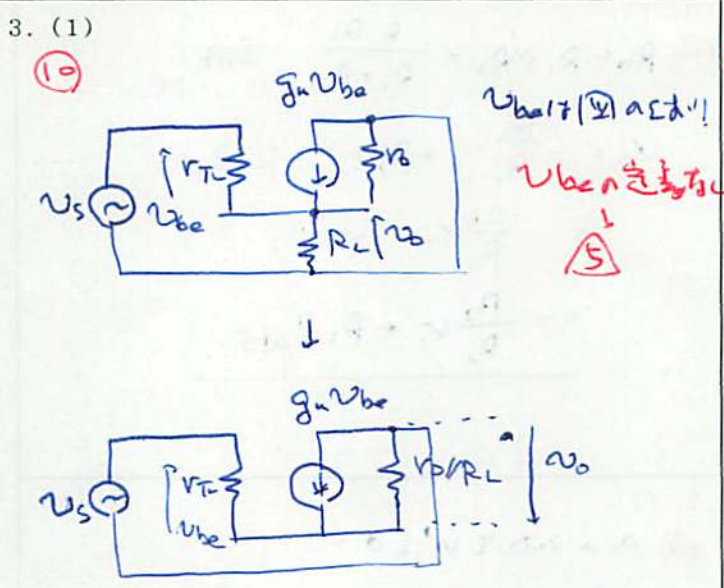

3. (2)

$$v_o = (r_o / R_L) g_m v_{be}$$

$$v_{be} = v_s - v_o$$

$$v_o = g_m (r_o / R_L) (v_s - v_o)$$

$$v_o (1 + g_m (r_o / R_L)) = g_m (r_o / R_L) v_s$$

$$\therefore \frac{v_o}{v_s} = A_v = \frac{g_m (r_o / R_L)}{1 + g_m (r_o / R_L)}$$

$\text{計算} \rightarrow \text{⑤}$

4. 基本的(1)(2)

たて.  $\text{計算} \rightarrow \text{⑤}$

(理想な非逆性回路の計算)